

# Audio Noise Gate: Technical Project Defense

## Project Documentation

### 1 Project Overview

This project implements an analog Audio Noise Gate designed to eliminate background noise from a single-supply audio system. The circuit utilizes an LM324 operational amplifier for signal processing and a CD4066 bilateral switch for gating. The system is designed to distinguish between human speech and background noise, effectively muting the audio output when the signal falls below a set threshold.

### 2 Circuit Analysis by Stage

#### 2.1 Virtual Ground Reference

**The Problem:** The circuit operates on a single supply (0V to 5V) derived from a USB or Arduino source. Audio signals are Alternating Current (AC) and naturally swing positive and negative. Without a reference, the negative half of the audio signal would be clipped at 0V (ground).

**The Solution:** A voltage divider creates a "Virtual Ground" at 2.5V, shifting the audio signal's center point to the middle of the supply range.

**Mathematical Derivation:** Using two equal resistors ( $R = 10k\Omega$ ):

$$V_{ref} = V_{supply} \times \frac{R}{R + R} = 5V \times \frac{10k\Omega}{20k\Omega} = 2.5V \quad (1)$$

This allows the audio signal to swing approximately  $\pm 2.5V$  relative to the virtual ground without clipping.

#### 2.2 Input Coupling & Stabilization

**Role of  $C_{IN}$  ( $10\mu F$ ): DC Blocking**

- **Purpose:** Acts as a bridge between the external audio source (centered at 0V) and the internal circuit (centered at 2.5V).
- **Function:** It blocks the 2.5V DC bias from flowing back into the microphone or phone (which could cause damage) while allowing the AC audio vibrations to pass through to the amplifier.

**Role of  $C_{BIAS}$  ( $10\mu F$  &  $100nF$ ): Voltage Stabilization**

- **Purpose:** These capacitors decouple the virtual ground reference from power supply fluctuations.
- **Mechanism:** They act as local energy reservoirs. When the Op-Amp draws current to drive a signal, these capacitors provide instantaneous charge, ensuring the 2.5V reference remains stable and does not "sag," effectively creating a solid "AC Ground."

## 2.3 2.3 Non-Inverting Amplifier

**Configuration:** A non-inverting topology was chosen to provide high input impedance, which prevents "loading down" the weak electret microphone signal.

**Gain Calculation:** With a feedback resistor ( $R_f$ ) of  $220k\Omega$  and a ground resistor ( $R_g$ ) of  $10k\Omega$ :

$$A_v = 1 + \frac{R_f}{R_g} = 1 + \frac{220k\Omega}{10k\Omega} = 1 + 22 = 23 \quad (2)$$

**Signal Levels:**

- **Input:**  $\approx 20mV$  (peak-to-peak)
- **Output:**  $20mV \times 23 = 460mV$  (peak-to-peak)

This amplification raises the weak microphone signal to a level usable for envelope detection.

## 2.4 2.4 Envelope Detection

**Purpose:** Converts the rapidly oscillating AC audio into a slowly-varying DC voltage that represents the "loudness" (amplitude) of the signal.

**Mechanism:** A diode rectifies the signal (passing only positive peaks), charging a capacitor. A parallel resistor discharges the capacitor during silence.

**Time Constant (Release Time):**

$$\tau = R \times C = 220k\Omega \times 2.2\mu F = 0.484 \text{ seconds} \quad (3)$$

**Justification:** A time constant of  $\approx 0.5s$  was selected to match natural speech patterns. Syllabic pauses typically last 100–300ms; a faster release would cause the gate to "chatter" (close) during these brief pauses, resulting in choppy audio.

## 2.5 2.5 Schmitt Trigger with Hysteresis

**The Problem:** A standard comparator with a single threshold suffers from "chatter" (rapid oscillation) when noisy signals hover near the threshold voltage.

**The Solution:** The Schmitt Trigger introduces hysteresis, creating two distinct thresholds:  $V_H$  (to turn ON) and  $V_L$  (to turn OFF).

**Hysteresis Width Calculation:** Given  $R_{in} = 10k\Omega$  and  $R_{feedback} = 2M\Omega$ :

$$\beta = \frac{R_{in}}{R_{in} + R_{feedback}} = \frac{10k\Omega}{10k\Omega + 2M\Omega} \approx 0.005 \quad (4)$$

$$V_{hyst} = \beta \times V_{supply} = 0.005 \times 5V = 25mV \quad (5)$$

This 25mV "dead zone" ensures the gate remains stable once opened, requiring a significant signal drop before closing.

## 2.6 2.6 CD4066 Bilateral Switch

**Component Choice:** The CD4066 is a digitally-controlled analog switch. Unlike transistors, it is "bilateral," meaning it passes AC signals in both directions without distortion.

**Attenuation Performance:** The measured attenuation in the OFF state is 30dB.

$$A_{off(dB)} = 20 \log_{10} \left( \frac{V_{out}}{V_{in}} \right) \quad (6)$$

Substituting 30dB:

$$30 = 20 \log_{10} \left( \frac{V_{in}}{V_{out}} \right) \implies \frac{V_{out}}{V_{in}} = 10^{-1.5} \approx 0.0316 \quad (7)$$

This indicates that only  $\approx 3.16\%$  of the noise signal leaks through when the gate is closed (a  $\approx 97\%$  reduction).

## 2.7 2.7 Sallen-Key Low-Pass Filter

**Purpose:** Removes high-frequency switching artifacts and digital noise introduced by the CD4066.

**Characteristics:**

- **Order:** Second-Order (-40dB/decade roll-off).
- **Advantage:** Provides a steep cutoff compared to first-order filters, effectively rejecting high-frequency noise while preserving voice frequencies.

**Cutoff Frequency:**

$$f_c = \frac{1}{2\pi\sqrt{R_1 R_2 C_1 C_2}} \quad (8)$$

Designed for 3–4kHz to accommodate the human voice spectrum.

# 3 Data Analysis & Results

## 3.1 Signal Behavior

- **Raw Input:** Clusters around -15dB during speech, dropping to -30dB to -35dB during silence (representing the noise floor).
- **Gated Output:** Effectively clamps the output during silence, preventing the deep excursions into the noise floor.

## 3.2 Performance Metrics

**Noise Floor Reduction:** 30dB.

$$10^{30/20} \approx 31.6 \quad (9)$$

The noise floor is reduced by a factor of approximately 32 times.

### 3.3 Leakage Explanation

The output does not reach absolute silence (-60dB or lower) due to **parasitic capacitance** within the CD4066 chip. This allows high-frequency signal components to "leak" across the open switch contacts, resulting in the measured -10dB floor rather than complete cutoff. This is a known limitation of solid-state analog switches compared to mechanical relays.

# Viva Voce: Audio Noise Gate Project Defense

## Candidate Responses

### 1 Fundamental Concept Questions

**Q1: Why did you choose a Schmitt Trigger instead of a regular comparator?**

**Answer:** A regular voltage comparator is extremely sensitive to noise. When an audio signal fluctuates or hovers near the reference threshold, a standard comparator's output would oscillate rapidly, causing the gate to open and close violently. This phenomenon is known as "chatter". We chose a Schmitt Trigger because it introduces *hysteresis*—two distinct voltage thresholds for turning ON and OFF—which stabilizes the detection and prevents this rapid switching.

**Q2: Explain the concept of hysteresis in your circuit.**

**Answer:** Hysteresis effectively creates a "dead zone" or a safety margin for the switching decision. Instead of a single tipping point, we have an Upper Threshold ( $V_H$ ) to open the gate and a Lower Threshold ( $V_L$ ) to close it. In our design, we calculated a hysteresis width of approximately 25mV. This means that once the gate opens, the signal amplitude must drop significantly (by 25mV) below the opening point before the gate will close again, ensuring the gate stays open during minor signal ripples.

**Q3: What is the purpose of the envelope follower?**

**Answer:** The noise gate needs to track the "loudness" of the signal, not the instantaneous frequency. The audio signal is AC (alternating positive and negative). The envelope follower rectifies this AC signal into a smooth DC voltage that rises and falls with the signal's overall amplitude. This allows the comparator to make a decision based on volume rather than the individual waveform peaks.

**Q4: Why is the virtual ground necessary?**

**Answer:** Our circuit runs on a single supply (0V to 5V) from the Arduino/USB. Audio signals are naturally AC and swing positive and negative. If we referenced the audio to true ground (0V), the negative half of the waveform would be clipped off (distorted). We use a voltage divider to create a "Virtual Ground" at 2.5V, which sits exactly in the middle of our supply, allowing the audio to swing up and down without hitting the voltage rails.

### **Q5: What does the Sallen-Key filter do in your design?**

**Answer:** The Sallen-Key filter acts as a "cleanup" stage at the very end of the signal chain. After the CD4066 switches the audio, there may be high-frequency switching artifacts or digital noise left in the signal. We implemented a Second-Order Low-Pass filter to aggressively remove frequencies above the voice band (3kHz), ensuring that the final signal going into the Arduino or speaker is clean and smooth.

## **2 Component-Specific Questions**

### **Q6: Why did you use CD4066 instead of a transistor or relay?**

**Answer:** We used the CD4066 because it is a "Bilateral Switch," meaning it allows current to flow in both directions. This is crucial for AC audio signals. A standard transistor is unidirectional (current flows only one way), which would rectify and distort the audio. A mechanical relay would be far too slow and noisy for this application. The CD4066 acts like a near-perfect resistor that can be digitally toggled.

### **Q7: What's the significance of the $2M\Omega$ feedback resistor in the Schmitt Trigger?**

**Answer:** The  $2M\Omega$  resistor ( $R_{feedback}$ ) is the key component that defines the hysteresis width. It creates a positive feedback loop from the output back to the input. The ratio between the input resistor ( $10k\Omega$ ) and this feedback resistor determines the feedback fraction ( $\beta$ ), which sets the "dead zone" to 25mV. If this resistor were removed, the circuit would revert to a noisy standard comparator.

### **Q8: Why did you choose the specific time constant for the envelope follower?**

**Answer:** We chose a time constant ( $\tau$ ) of approximately 0.48 seconds. This is the "Release Time." It matches the natural rhythm of human speech. When we speak, there are small gaps (100-300ms) between syllables. If the release time were faster, the gate would shut instantly during these gaps, making the voice sound choppy or robotic. The 0.5s delay holds the gate open just long enough to bridge these gaps.

### **Q9: What's the role of the LM324 vs LM393 in your circuit?**

**Answer:** The LM324 is an Operational Amplifier (Op-Amp) used for analog signal conditioning—specifically amplification and filtering. The LM393 is a dedicated Voltage Comparator used for the logic decision (High/Low) of the Schmitt Trigger. While an Op-Amp \*can\* act as a comparator, the LM393 is designed specifically for fast switching digital outputs, which is why we separated the roles.

### 3 Troubleshooting Questions

#### Q10: What challenges did you face during implementation?

**Answer:** We faced three main challenges:

1. **Comparator Chatter:** Solved by adding hysteresis (Schmitt Trigger).
2. **Floating Output Noise:** The switch output acted as an antenna when open, picking up 50Hz mains hum.
3. **Power Supply Noise:** Digital noise from the Arduino affected the audio, which we solved with decoupling capacitors.

#### Q11: What is the pull-down resistor for, and why 10kΩ?

**Answer:** The 10kΩ resistor at the switch output forms a "Pull-Down Network". When the CD4066 switch opens (turns OFF), the output wire is technically disconnected (floating). Without the resistor, this floating wire picks up electromagnetic interference (hum). The resistor drains any stray charge to ground (0V) immediately, ensuring the output is silent.

#### Q12: How does the decoupling capacitor help?

**Answer:** We placed a 100μF capacitor near the power pins of the LM324. Since the sensitive audio circuit shares a 5V power rail with the noisy digital Arduino, the capacitor acts as a local energy reservoir. It absorbs voltage spikes and fills in dips, ensuring the Op-Amp receives a smooth, steady power supply.

### 4 Design Calculation Questions

#### Q13: Calculate the gain of your pre-amplifier.

**Answer:** The gain ( $A_v$ ) for a non-inverting amplifier is calculated as:

$$A_v = 1 + \frac{R_f}{R_g} \quad (1)$$

Using our values of  $R_f = 220k\Omega$  and  $R_g = 10k\Omega$ , the gain is  $1 + 22 = 23$ .

#### Q14: Show how you calculated the hysteresis width.

**Answer:** The hysteresis is determined by the feedback fraction  $\beta$ :

$$\beta = \frac{R_{in}}{R_{in} + R_{feedback}} = \frac{10k\Omega}{10k\Omega + 2M\Omega} \approx 0.005 \quad (2)$$

The voltage width is then derived from the supply voltage:

$$V_{hyst} = \beta \times V_{supply} = 0.005 \times 5V = 25mV \quad (3)$$

This confirms our 25mV dead zone.

### Q15: What is the cutoff frequency of your Sallen-Key filter?

**Answer:** The cutoff frequency formula for this topology is:

$$f_c = \frac{1}{2\pi\sqrt{R_1 R_2 C_1 C_2}} \quad (4)$$

We selected components to target a cutoff of approximately  $3kHz$ , which isolates the human voice band while rejecting higher frequency noise.

## 5 Performance Questions

### Q16: What does 30dB noise reduction mean in practical terms?

**Answer:** Decibels are logarithmic. A 30dB reduction is calculated as a voltage ratio of:

$$10^{30/20} \approx 31.6 \quad (5)$$

This means the background noise is approximately 32 times quieter when the gate is closed compared to when it is open. It represents a massive, clearly audible improvement in signal quality.

### Q17: Why doesn't the gated output go to -60dB (silence) when the gate is closed?

**Answer:** In a perfect world, it would. However, the CD4066 is a real-world component with "parasitic capacitance." Even when the internal switch is open, high-frequency signals can slightly "leak" across the open contacts. Our data shows the floor drops significantly but sits around -10dB to -12dB relative to our plot scale rather than absolute zero, due to this leakage.

### Q18: How do you know there's no 'chatter' in your system?

**Answer:** We verified this via our Python data logs. The graph of the "Gated Output" shows a stable, flat line during silence. If chatter were present, we would see rapid, vertical spikes in the graph as the gate frantically opened and closed. The stability of the output trace confirms the hysteresis is working correctly.

## 6 Advanced/Conceptual Questions

### Q19: Could you implement this digitally? What would be the trade-offs?

**Answer:** Yes, this could be done in software (DSP).

- **Digital Advantage:** Easier to tune thresholds perfectly without changing resistors.
- **Digital Disadvantage:** Latency. The signal must be converted to digital (ADC), processed, and converted back (DAC), which takes time. Our analog circuit operates in real-time with effectively zero latency.



**Q20: What improvements would you suggest for a production version?**

**Answer:**

1. Use a specialized audio switch chip with lower leakage than the CD4066 (improving the 30dB attenuation).
2. Use a dual-rail power supply ( $+5V/-5V$ ) to eliminate the need for a virtual ground, which simplifies biasing and increases headroom.
3. Implement a PCB layout with separate analog and digital ground planes to further reduce noise.

**Q21: Explain how your Python/Arduino code verifies the circuit performance.**

**Answer:** The Arduino acts as a high-speed data logger, reading both the "Raw Input" and "Gated Output" voltages simultaneously. We optimized the Arduino ADC prescaler to sample fast enough for audio. The Python script then reads this serial data, converts the voltage levels into Decibels (dB), and plots them in real-time. This allowed us to visually confirm that when the input dropped to -35dB (noise), the output remained clamped, providing empirical proof of the gate's function.